

**The University of Jordan  
School of Engineering  
Electrical Engineering Department**

**EE 449  
Instrumentation and Control Lab**

**EXPERIMENT 4 REPORT  
ELECTROPNEUMATIC CONTROL SYSTEMS**

Section # \_\_\_\_\_ Group # \_\_\_\_\_

**Student Name**

**ID**

- 1.
- 2.
- 3.
- 4.

## EXPERIMENT 4 ELECTROPNEUMATIC CONTROL SYSTEMS

### PROCEDURE 1 – Direct control of single-acting cylinder from two different locations

4. Connect the system and record your results in the following table:

x1	x2	OR gate output (expected)	a0	a1	Cylinder status
0	0				
0	1				
0	0				
1	0				
0	0				
1	1				
0	0				

5. Explain what happened when you reset control signals  $x1 = x2 = 0$  after each step.

.....  
 .....

6. Slow down the flow air speed manually by the related valve and repeat the previous step. What did you notice?

.....  
 .....

### PROCEDURE 2 – Indirect control of a double acting cylinder by a single pushbutton

4. Connect the system and record your results in the following table:

x	a0	a1	Cylinder status
1			
0			

5. Explain what happened.

.....

.....

.....

.....

**PROCEDURE 3 – Semiautomatic control of double acting cylinder by a limit switch without and with Timed return**

3. Put the control signal (pushbutton inputs) (Primary Moving Switch (PMS)=1).

4. Explain what happened.

.....

.....

.....

.....

.....

.....

6. Modify the previous control system as shown in fig (1.22). What do you expect the mode of this timer to be? (NC or NO).

.....

.....

9. Put the control signal (pushbutton inputs) (PMS=1).

10. Explain how this system works.

.....

.....

.....  
.....  
.....  
.....  
.....  
.....

11. Modify the above timed return control system such that A+ and A- are repeated automatically indefinitely. (Hint: connect a0 and pushbutton to suitable logic gate). Explain how your system works.

.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....  
.....

12. Draw the electronic diagram of your control system.

.....  
.....  
.....  
.....  
.....  
.....

**PROCEDURE 4 – A control System of two double acting cylinders**

5. Connect the system and record your results in the following table:

<b>Phase #</b>	<b>a0</b>	<b>a1</b>	<b>A</b>	<b>b0</b>	<b>b1</b>	<b>B</b>
1						
2						
3						
4						
5						
6						

6. How many times the phases will be repeated? Explain why.

.....

.....

.....

.....

.....

.....

.....

.....

.....

7. Turn the lever OFF. What will happen? Explain.

.....

.....

.....

.....

8. What will change if you replace the lever valve with pushbutton valve?

.....  
.....  
.....  
.....

9. What is the effect of the initial value of a0 in this control design?

.....  
.....  
.....  
.....

**PROCEDURE 5 – (5) Electronic control System**

3. Connect the system and record your results in the following table:

A	B	U
0	0	
0	1	
1	0	
1	1	

4. State the equivalent logic function of this logical control system.

$$U =$$

5. What is the equivalent logic gate of this function?

.....

**PROCEDURE 6 (I) – Electropneumatic control System, First example**

5. What is the state of a1 when you start?

.....

6. Explain what happen to each part of the system at all phases.

.....

.....

.....

.....

.....

.....

.....

**PROCEDURE 6 (II) – Electropneumatic control System, Second example**

6. What is the initial value of a0, a1, b0 and b1?

.....

.....

.....

.....

8. Explain what happen to each part of the system at all phases.

.....

.....

.....

.....

.....

.....

.....

10. Show the electronic diagram of the following functions.

$$\bar{A}B$$

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

$$\bar{B} + \bar{C}$$

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

**\*\* End \*\***